
 
 


PROGRAMMABLE LOGIC DEVICES

 


PLDs (combinatorial circuits): ROM, PLA, PAL, CPLD, and FPGA

Store *permanent* binary information (nonvolatile). Can be read only (cannot be altered). Information is specified by designer and *physically inserted* (embedded) into the PLD

Programmable connections are formed by *fuses*, *masks*, or *antifuses* depending on the technology. Irreversible programming

Read-Only Memory

 k inputs
(address) $\Rightarrow$ $2^k \times n$ ROM $\Rightarrow$ n outputs
(data)



- $k \times 2^k$ decoder to decode input address
- n OR gates with 2^k input each
- Decoder output is connected to all n OR gates through fuses
- ROM $\rightarrow 2^k \times n$ programmable connections


Programming a ROM

Example of 4×2 ROM


Truth table

Address		Content	
I_1	I_0	A_1	A_0
0	0	0	1
0	1	1	0
1	0	1	1
1	1	1	0


NonProgrammed ROM

 

Programmed ROM

 

Compact ROM

 

Truth table → address and content of ROM


Programming → stores truth table in ROM

- 0 = Open connection = Fuse blown
- 1 = Closed connection = Fuse intact


Function Synthesis with ROM

Any set of functions $f_1(x_k, \dots, x_1), \dots, f_n(x_k, \dots, x_1)$ can be realized with a $2^k \times n$ ROM

 Example: Implement $f_1(x_2, x_1) = \sum m(0, 3)$,
 $f_2(x_2, x_1) = \overline{x_2 + x_1}$, and $f_3(x_2, x_1) = \prod M(1)$ with a 4×3 ROM



Programmable Logic Array

 


Behave like a ROM but has different structure

- Uses ANDs array instead of decoder to produce product terms of inputs
- Has programmable connections before ANDs, between ANDs and ORs, after ORs. That is $2nk + km + m$ fuses
- More flexible than ROM but more difficult to program
- Logic expressions for content information to be stored in PLA must be obtained first, then minimized, and finally programmed into the PLA using a PLA program table
- PLA program table specifies product terms and sum terms of information that will be stored in PLA

Programming a PLA

PLA Program Table						
Term	Term#	Inputs			Outputs	
		A	B	C	F_1	F_2
$A\bar{B}$	1	1	0	–	1	–
AC	2	1	–	1	1	1
BC	3	–	1	1	–	1
$\bar{A}B\bar{C}$	4	0	1	0	1	–
					T	C

 

Function Synthesis with PLA

Any set of functions $f_1(x_1, \dots, x_n), \dots, f_m(x_1, \dots, x_n)$ can be realized with a PLA

Example Implement $f_1(a, b, c) = \sum m(3, 5, 6, 7)$ and $f_2(a, b, c) = \sum m(0, 2, 4)$ with a PLA

First Simplify $f_1, \bar{f}_1, f_2, \bar{f}_2$, that is

$$\begin{array}{ll} f_1(a, b, c) = ab + ac + bc & f_1, f_2 \rightarrow 5 \text{ terms} \\ \bar{f}_1(a, b, c) = \bar{a}\bar{b} + \bar{a}\bar{c} + \bar{b}\bar{c} & f_1, \bar{f}_2 \rightarrow 4 \text{ terms} \\ f_2(a, b, c) = \bar{a}\bar{c} + \bar{b}\bar{c} & \bar{f}_1, f_2 \rightarrow 3 \text{ terms} \\ \bar{f}_2(a, b, c) = ab + c & \bar{f}_1, \bar{f}_2 \rightarrow 5 \text{ terms} \end{array}$$

Second Select combination of functions that has less terms, that is

$$\begin{array}{l} f_1 = \bar{f}_1 = \bar{a}\bar{b} + \bar{a}\bar{c} + \bar{b}\bar{c} \\ f_2(a, b, c) = \bar{a}\bar{c} + \bar{b}\bar{c} \end{array}$$

Third Construct a PLA program table from selected functions

		Inputs			Outputs	
Term	Term#	a	b	c	f_1	f_2
$\bar{a}\bar{b}$	1	0	0	–	1	–
$\bar{a}\bar{c}$	2	0	–	0	1	1
$\bar{b}\bar{c}$	3	–	0	0	1	1
					C	T


Function Synthesis with PLA

(continued)


Third Construct a PLA program table from selected functions

Term	Term#	Inputs			Outputs	
		a	b	c	f_1	f_2
$\bar{a}\bar{b}$	1	0	0	–	1	–
$\bar{a}\bar{c}$	2	0	–	0	1	1
$\bar{b}\bar{c}$	3	–	0	0	1	1
					C	T

 Fourth Construct PLA circuit from PLA program table




Programmable Array Logic

 


Similar to PLA

- Only the connection inputs to ANDs are programmable
- Easier to program than but not as flexible as PLA
- There are feedback connections
- Logic expressions for content information to be stored in PAL must be obtained first, then minimized, and finally programmed into the PAL using a PAL program table
- PAL program table specifies only product terms of information that will be stored in PAL

Programming a PAL

 

Arithmetic-Logic Unit

 

Essential element of the Central Processing Unit


Arithmetic and logic functions on binary words

- n -bit data inputs A and B
- n -bit data output $G = f(A, B)$
- Selection inputs S_0, S_1 select a function f
- Selection input S_2 select an operating mode (arithmetic or logic)

ALU

(continued)

Logic Circuit

 


(a) Logic Diagram

S_1	S_0	Output	Operation
0	0	$G = A \wedge B$	AND
0	1	$G = A \vee B$	OR
1	0	$G = A \oplus B$	XOR
1	1	$G = \bar{A}$	NOT


(b) Function Table

Arithmetic Circuit

 

ALU

(continued)

 

ALU

(continued)

