

SWITCHING ALGEBRA

$$\text{Algebra} = \begin{cases} \text{Elements} = B = \{0, 1\} \\ + \\ \text{Operators} = \{\text{OR}, \text{AND}, \text{NOT}\} \end{cases}$$

Properties of Boolean algebra

1a. $x + 0 = x$	1b. $x \cdot 1 = x$	Identity element
2a. $x + 1 = 1$	2b. $x \cdot 0 = 0$	Universal bound
3a. $x + x = x$	3b. $x \cdot x = x$	Idempotency
4a. $x + \bar{x} = 1$	4b. $x \cdot \bar{x} = 0$	Complementation
5. $\bar{\bar{x}} = x$		Involution

6a. $x + y = y + x$	Commutativity
6b. $x \cdot y = y \cdot x$	
7a. $x + (y + z) = (x + y) + z$	Associativity
7b. $x \cdot (y \cdot z) = (x \cdot y) \cdot z$	
8a. $x \cdot (y + z) = (x \cdot y) + (x \cdot z)$	Distributivity
8b. $x + (y \cdot z) = (x + y) \cdot (x + z)$	
9a. $\overline{x + y} = \bar{x} \cdot \bar{y}$	DeMorgan's law
9b. $\overline{x \cdot y} = \bar{x} + \bar{y}$	
10a. $x + (x \cdot y) = x$	Absorption
10b. $x \cdot (x + y) = x$	
11a. $(x \cdot y) + (x \cdot \bar{y}) = x$	Combining
11b. $(x + y) \cdot (x + \bar{y}) = x$	
12a. $x + y = x + z \Rightarrow y = z$	Non-Cancellation
12b. $x \cdot y = x \cdot z \Rightarrow y = z$	
13a. $x + (\bar{x} \cdot y) = x + y$	No name?
13b. $x \cdot (\bar{x} + y) = x \cdot y$	

Where $+$ = OR, $\cdot$ = AND, $\bar{}$ = NOT

Switching Functions $f: \{0, 1\}^n \mapsto \{0, 1\}$

f is a function of n variables $x_1, \dots, x_n$ such that

$$\begin{cases} x_i & \in \{0, 1\}, \quad 1 \leq i \leq n \\ f(x_1, \dots, x_n) & \in \{0, 1\} \end{cases}$$

Any Boolean function f can be specified either by

Truth table

Row#		x_1	x_2	$\dots$	x_{n-1}	x_n	f
0	$\mapsto$	0	0	$\dots$	0	0	-
1	$\mapsto$	0	0	$\dots$	0	1	-
$\vdots$	$\vdots$	$\vdots$	$\vdots$	$\vdots$	$\vdots$	$\vdots$	$\vdots$
$2^n - 2$	$\mapsto$	1	1	$\dots$	1	0	-
$2^n - 1$	$\mapsto$	1	1	$\dots$	1	1	-

There are 2^n combinations of 0's and 1's.

Boolean expression e such that $f(x_1, \dots, x_n) = e$ where e is either a Boolean constant, a Boolean variable, or any expression that contains constants, variables or Boolean operators. Examples:












$$f(x_1, x_2, x_3) = (x_1 \oplus x_3) \cdot \bar{x}_2 + 1$$

$$f(x_1, x_2) = x_1$$

$$f(x_1, x_2, x_3, x_4) = 0$$

Boolean algebra is used to simplify and minimize Boolean expressions for given Boolean functions

Basic Switching Functions (Logic Gates)

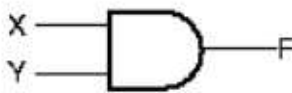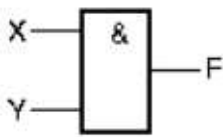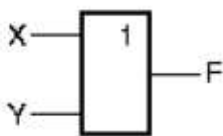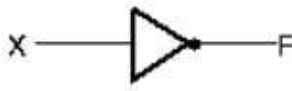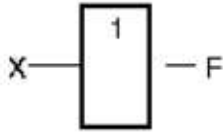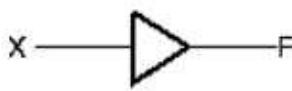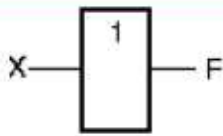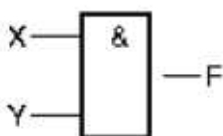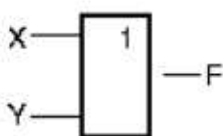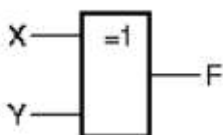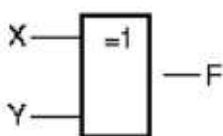Name	Distinctive shape	Rectangular shape	Algebraic equation	Truth table															
AND			$F = XY$	<table><tr><th>X</th><th>Y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	X	Y	F	0	0	0	0	1	0	1	0	0	1	1	1
X	Y	F																	
0	0	0																	
0	1	0																	
1	0	0																	
1	1	1																	
OR			$F = X + Y$	<table><tr><th>X</th><th>Y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	X	Y	F	0	0	0	0	1	1	1	0	1	1	1	1
X	Y	F																	
0	0	0																	
0	1	1																	
1	0	1																	
1	1	1																	
NOT (inverter)			$F = \bar{X}$	<table><tr><th>X</th><th>F</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	X	F	0	1	1	0									
X	F																		
0	1																		
1	0																		
Buffer			$F = X$	<table><tr><th>X</th><th>F</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	X	F	0	0	1	1									
X	F																		
0	0																		
1	1																		
NAND			$F = \overline{X \cdot Y}$	<table><tr><th>X</th><th>Y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	X	Y	F	0	0	1	0	1	1	1	0	1	1	1	0
X	Y	F																	
0	0	1																	
0	1	1																	
1	0	1																	
1	1	0																	
NOR			$F = \overline{X + Y}$	<table><tr><th>X</th><th>Y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	X	Y	F	0	0	1	0	1	0	1	0	0	1	1	0
X	Y	F																	
0	0	1																	
0	1	0																	
1	0	0																	
1	1	0																	
Exclusive-OR (XOR)			$F = X\bar{Y} + \bar{X}Y$ $= X \oplus Y$	<table><tr><th>X</th><th>Y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	X	Y	F	0	0	0	0	1	1	1	0	1	1	1	0
X	Y	F																	
0	0	0																	
0	1	1																	
1	0	1																	
1	1	0																	
Exclusive-NOR (XNOR)			$F = XY + \bar{X}\bar{Y}$ $= \overline{X \oplus Y}$	<table><tr><th>X</th><th>Y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	X	Y	F	0	0	1	0	1	0	1	0	0	1	1	1
X	Y	F																	
0	0	1																	
0	1	0																	
1	0	0																	
1	1	1																	

Algebraic Simplifications

(Reduce the length of a Boolean expression)

Simplify $f(x_1, x_2, x_3) = x_1\bar{x}_3 + \bar{x}_1x_2 + \bar{x}_1\bar{x}_2\bar{x}_3$

$$\begin{array}{ll}
 x_1\bar{x}_3 + \underbrace{\bar{x}_1x_2 + \bar{x}_1x_2\bar{x}_3 + \bar{x}_1\bar{x}_2\bar{x}_3}_{\text{Absorption}} & \\
 x_1\bar{x}_3 + \bar{x}_1x_2 + \underbrace{\bar{x}_1\bar{x}_3(x_2 + \bar{x}_2)}_{\text{Distributivity}} & \\
 x_1\bar{x}_3 + \bar{x}_1x_2 + \underbrace{\bar{x}_1\bar{x}_3(1)}_{\text{Complementation}} & \\
 x_1\bar{x}_3 + \bar{x}_1x_2 + \underbrace{\bar{x}_1\bar{x}_3}_{\text{Identity element}} & \\
 \underbrace{\bar{x}_1x_2 + x_1\bar{x}_3}_{\text{Commutativity}} + \bar{x}_1\bar{x}_3 & \\
 \bar{x}_1x_2 + \underbrace{\bar{x}_3x_1 + \bar{x}_3\bar{x}_1}_{\text{Commutativity}} & \\
 \bar{x}_1x_2 + \bar{x}_3 \underbrace{(x_1 + \bar{x}_1)}_{\text{Distributivity}} & \\
 \bar{x}_1x_2 + \bar{x}_3 \underbrace{(1)}_{\text{Complementation}} & \\
 \Rightarrow f(x_1, x_2, x_3) = \bar{x}_1x_2 + \underbrace{\bar{x}_3}_{\text{Identity element}} &
 \end{array}$$

Simplify $f(x_1, x_2, x_3) = x_1\bar{x}_3 + \bar{x}_2\bar{x}_3 + x_1x_3 + \bar{x}_2x_3$

$$\begin{array}{ll}
 x_1\bar{x}_3 + \underbrace{x_1x_3 + \bar{x}_2\bar{x}_3}_{\text{Commutativity}} + \bar{x}_2x_3 & \\
 \underbrace{x_1(\bar{x}_3 + x_3)}_{\text{Distributivity}} + \underbrace{\bar{x}_2(\bar{x}_3 + x_3)}_{\text{Distributivity}} & \\
 x_1 \underbrace{(1)}_{\text{Complementation}} + \bar{x}_2 \underbrace{(1)}_{\text{Complementation}} & \\
 \Rightarrow f(x_1, x_2, x_3) = \underbrace{x_1}_{\text{Identity element}} + \underbrace{\bar{x}_2}_{\text{Identity element}} &
 \end{array}$$

Simplify

$$f(x_1, x_2) = \bar{x}_1\bar{x}_2 + x_1x_2 + x_1\bar{x}_2$$

$$f(x_1, x_2, x_3) = x_1 + x_1x_2x_3 + \bar{x}_1x_3$$

$$f(x_1, x_2, x_3) = (x_1 + \bar{x}_2 + x_1\bar{x}_2)(x_1x_2 + \bar{x}_1x_3 + x_2x_3)$$

$$f(x_1, x_2, x_3, x_4) = (x_2\bar{x}_3 + \bar{x}_1x_4)(x_1\bar{x}_2 + x_3\bar{x}_4)$$

Demonstrations

(Are two Boolean expressions equivalent?)

Algebraic demonstration

$$(x_1 + x_3)(\bar{x}_1 + \bar{x}_3) \stackrel{?}{=} x_1\bar{x}_3 + \bar{x}_1x_3$$

LHS =

$$(x_1 + x_3)\bar{x}_1 + (x_1 + x_3)\bar{x}_3$$

Distributivity

$$x_1\bar{x}_1 + x_3\bar{x}_1 + x_1\bar{x}_3 + x_3\bar{x}_3$$

Distributivity

$$0 + x_3\bar{x}_1 + x_1\bar{x}_3 + 0$$

Complementation

$$x_3\bar{x}_1 + x_1\bar{x}_3$$

Identity element

$$x_1\bar{x}_3 + \bar{x}_1x_3$$

Commutativity

= RHS

Tabular demonstration

$$\overline{x \cdot y} \stackrel{?}{=} \bar{x} + \bar{y}$$

x	y	$\bar{x}$	$\bar{y}$	$x \cdot y$	$\overline{x \cdot y}$	$\bar{x} + \bar{y}$
0	0	1	1	0	1	1
0	1	1	0	0	1	1
1	0	0	1	0	1	1
1	1	0	0	1	0	0
LHS					RHS	

What are the advantages of algebraic demonstration over tabular demonstration and vice-versa?

Minterms and Maxterms

In truth table of $f(x_1, \dots, x_n)$ each combination of 0's and 1's can be represented as a

Minterm $l_1 \cdot l_2 \cdot \dots \cdot l_n$ (product term)
 $= 0$ if a least one literal is 0

Maxterm $l_1 + l_2 + \dots + l_n$ (sum term)
 $= 1$ if a least one literal is 1

where *literal* $l_i = x_i$ or $\bar{x}_i$, for $1 \leq i \leq n$

3-variable minterms and maxterms

Row	x_1	x_2	x_3	Minterm	Maxterm
0	0	0	0	$m_0 : \bar{x}_1 \bar{x}_2 \bar{x}_3$	$M_0 : x_1 + x_2 + x_3$
1	0	0	1	$m_1 : \bar{x}_1 \bar{x}_2 x_3$	$M_1 : x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 : \bar{x}_1 x_2 \bar{x}_3$	$M_2 : x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 : \bar{x}_1 x_2 x_3$	$M_3 : x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 : x_1 \bar{x}_2 \bar{x}_3$	$M_4 : \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 : x_1 \bar{x}_2 x_3$	$M_5 : \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 : x_1 x_2 \bar{x}_3$	$M_6 : \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 : x_1 x_2 x_3$	$M_7 : \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

$$\text{DeMorgan's law} \Rightarrow \begin{cases} \bar{m}_i = M_i \\ \bar{M}_i = m_i \end{cases} \text{ for } 1 \leq i \leq n$$

Note: not all product terms (respectively, sum terms) are minterms (respectively, maxterms)

Canonical Forms

Any function $f(x_1, \dots, x_n)$ can be expressed as a

Canonical sum of products: (CSOP) Sum of minterms for which f has value 1

$$f(x_1, \dots, x_n) = \sum_{i=0}^{2^n-1} (\alpha_i \cdot m_i)$$

Canonical product of sums: (CPOS) Product of maxterms for which f has value 0

$$f(x_1, \dots, x_n) = \prod_{i=0}^{2^n-1} (\alpha_i + M_i)$$

where α_i ($1 \leq i \leq 2^n - 1$) is the value of f

Example if $f(x_1, x_2) = x_1 \oplus x_2$ then

CSOP: $f(x_1, x_2) = m_1 + m_2 = \sum m(1, 2)$

$$0\bar{x}_1\bar{x}_2 + 1\underbrace{\bar{x}_1x_2}_{m_1} + 1\underbrace{x_1\bar{x}_2}_{m_2} + 0x_1x_2$$

CPOS: $f(x_1, x_2) = M_0 \cdot M_3 = \prod M(0, 3)$

$$(0 + \underbrace{x_1 + x_2}_{M_0})(1 + x_1 + \bar{x}_2)(1 + \bar{x}_1 + x_2)(0 + \underbrace{\bar{x}_1 + \bar{x}_2}_{M_3})$$

Examples of Canonical Forms

$$f(x_1, x_2, x_3) = \overline{x_1 \oplus x_2 \oplus x_3}$$

#	x_1	x_2	x_3	Minterm	Maxterm	f
0	0	0	0	$\bar{x}_1\bar{x}_2\bar{x}_3$	$x_1 + x_2 + x_3$	1
1	0	0	1	$\bar{x}_1\bar{x}_2x_3$	$x_1 + x_2 + \bar{x}_3$	0
2	0	1	0	$\bar{x}_1x_2\bar{x}_3$	$x_1 + \bar{x}_2 + x_3$	0
3	0	1	1	$\bar{x}_1x_2x_3$	$x_1 + \bar{x}_2 + \bar{x}_3$	1
4	1	0	0	$x_1\bar{x}_2\bar{x}_3$	$\bar{x}_1 + x_2 + x_3$	0
5	1	0	1	$x_1\bar{x}_2x_3$	$\bar{x}_1 + x_2 + \bar{x}_3$	1
6	1	1	0	$x_1x_2\bar{x}_3$	$\bar{x}_1 + \bar{x}_2 + x_3$	1
7	1	1	1	$x_1x_2x_3$	$\bar{x}_1 + \bar{x}_2 + \bar{x}_3$	0



CSOP:

$$f(x_1, x_2, x_3) = m_0 + m_3 + m_5 + m_6 = \sum m(0, 3, 5, 6) = \bar{x}_1\bar{x}_2\bar{x}_3 + \bar{x}_1x_2x_3 + x_1\bar{x}_2x_3 + x_1x_2\bar{x}_3$$

CPOS:

$$f(x_1, x_2, x_3) = M_1 \cdot M_2 \cdot M_4 \cdot M_7 = \prod M(1, 2, 4, 7) = (x_1 + x_2 + \bar{x}_3)(x_1 + \bar{x}_2 + x_3)(\bar{x}_1 + x_2 + x_3)(\bar{x}_1 + \bar{x}_2 + \bar{x}_3)$$

Equivalence of forms CSOP $\xleftrightarrow{\quad}$ CPOS conversions

1. Interchange symbols $\sum$ and $\prod$
2. List those numbers missing in the original

Example from above

$$\sum m(0, 3, 5, 6) = \prod M(1, 2, 4, 7)$$

Standard Forms

Sum of products: (SOP) Not all product terms are minterms

$$f(x_1, x_2, x_3) = \bar{x}_1x_2 + \bar{x}_3 + x_1x_2x_3$$

Product of sums: (POS) Not all sum terms are maxterms

$$f(x_1, x_2, x_3) = (\bar{x}_1)(\bar{x}_2 + x_3)$$

From standard form to canonical form

SOP $\mapsto$ CSOP For each missing variable x_i in a term t perform $(x_i + \bar{x}_i) \cdot t$. Then simplify and eliminate redundant minterms

$$\begin{aligned} \text{EX: } f(x_1, x_2, x_3) &= \bar{x}_1x_2 + \bar{x}_3 + x_1x_2x_3 \\ &= \bar{x}_1x_2(x_3 + \bar{x}_3) + (x_1 + \bar{x}_1)(x_2 + \bar{x}_2)\bar{x}_3 + x_1x_2x_3 \\ &= \bar{x}_1x_2x_3 + \bar{x}_1x_2\bar{x}_3 + x_1x_2\bar{x}_3 + x_1\bar{x}_2\bar{x}_3 + \bar{x}_1x_2\bar{x}_3 + \bar{x}_1\bar{x}_2\bar{x}_3 + x_1x_2x_3 \\ &= \bar{x}_1x_2x_3 + \bar{x}_1x_2\bar{x}_3 + x_1x_2\bar{x}_3 + x_1\bar{x}_2\bar{x}_3 + \bar{x}_1\bar{x}_2\bar{x}_3 + x_1x_2x_3 \\ &= m_3 + m_2 + m_6 + m_4 + m_0 + m_7 \\ &= \sum m(0, 2, 3, 4, 6, 7) = \text{CSOP } f(x_1, x_2, x_3) \end{aligned}$$

POS $\mapsto$ CPOS For each missing variable x_i in a term t perform $(x_i \cdot \bar{x}_i) + t$. Then simplify and eliminate redundant maxterms

Remarks on Logic Functions

Uniqueness The CSOP or CPOS of a logic function is unique

Equivalence $f_1 = f_2 \Leftrightarrow \begin{cases} \text{CSOP } f_1 = \text{CSOP } f_2 \\ \text{or} \\ \text{CPOS } f_1 = \text{CPOS } f_2 \end{cases}$

Number of n -variable switching functions 2^{2^n}

Ex: there are 2^{2^2} 2-variable switching functions

Truth tables of 16 functions of two variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7
0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1
Op.			$\cdot$	$/$		$/$		$\oplus$	$+$

x	y	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1
Op.		$\downarrow$	$\sim$	$-$	$\rightarrow$	$-$	$\rightarrow$	$\uparrow$	

Two-Variable Switching Functions

Function	Op.	Name	Comment
$F_0 = 0$		Null	constant 0
$F_1 = xy$	$x \cdot y$	AND	x and y
$F_2 = x\bar{y}$	x/y	Inhibition	x but not y
$F_3 = x$		Transfer	x
$F_4 = \bar{x}y$	y/x	Inhibition	y but not x
$F_5 = y$		Transfer	y
$F_6 = x\bar{y} + \bar{x}y$	$x \oplus y$	Exclusive-OR	either x or y
$F_7 = x + y$	$x \uparrow y$	OR	x or y
$F_8 = \overline{x + y}$	$x \downarrow y$	NOR	Not-OR
$F_9 = xy + \bar{x}\bar{y}$	$x \sim y$	Exclusive-NOR	x equals y
$F_{10} = \bar{y}$	$\bar{y}$	Complement	Not y
$F_{11} = x + \bar{y}$	$y \rightarrow x$	Implication	if y then x
$F_{12} = \bar{x}$	$\bar{x}$	Complement	Not x
$F_{13} = \bar{x} + y$	$x \rightarrow y$	Implication	if x then y
$F_{14} = \overline{xy}$	$x \uparrow y$	NAND	Not-AND
$F_{15} = 1$		Identity	constant 1

Exclusive-NOR is also known as *Equality*, *Coincidence* or *Equivalence*

From canonical form to standard form

- By algebraic simplification (as in slide #4)
- By graphical simplification (we'll see soon)

Functional Completeness

A set F of operators is *functionally complete* if and only if any Boolean function $f: \{0, 1\}^n \mapsto \{0, 1\}$ can be expressed using operators from F only

$F = \{\mathbf{OR}, \mathbf{AND}, \mathbf{NOT}\}$ is functionally complete (?)

$F = \{\mathbf{NOR}\}$ is functionally complete

$$\mathbf{OR} : x + y = \overline{\overline{x + y}} = \overline{\overline{x} \cdot \overline{y}} = (x \downarrow y) \downarrow 0$$

$$\mathbf{AND} : x \cdot y = \overline{\overline{x} + \overline{y}} = (x \downarrow 0) \downarrow (y \downarrow 0)$$

$$\mathbf{NOT} : \bar{x} = \overline{x + 0} = x \downarrow 0$$

$F = \{\mathbf{NAND}\}$ is functionally complete

$$\mathbf{OR} : x + y = \overline{\overline{x} \cdot \overline{y}} = (x \uparrow 1) \uparrow (y \uparrow 1)$$

$$\mathbf{AND} : x \cdot y = \overline{\overline{x} + \overline{y}} = \overline{\overline{x} \cdot \overline{y} \cdot 1} = (x \uparrow y) \uparrow 1$$

$$\mathbf{NOT} : \bar{x} = \overline{x \cdot 1} = x \uparrow 1$$

Example

$$\begin{aligned} f(x, y, z) &= (x + y)(\bar{y} + z) = \overline{\overline{x + y} + \overline{\bar{y} + z}} \\ &= (x \downarrow y) \downarrow (\bar{y} \downarrow z) \end{aligned}$$


$$f(x, y, z) = xy + \bar{y}z = \overline{\overline{xy} \cdot \overline{\bar{y}z}} = (x \uparrow y) \uparrow (\bar{y} \uparrow z)$$

Switching Circuits


Implement (or realize) switching functions

- Expression $\mapsto$ Circuit
- Term $\mapsto$ Gate
- Literal $\mapsto$ Input to gates

Functions can be realized in *many ways*

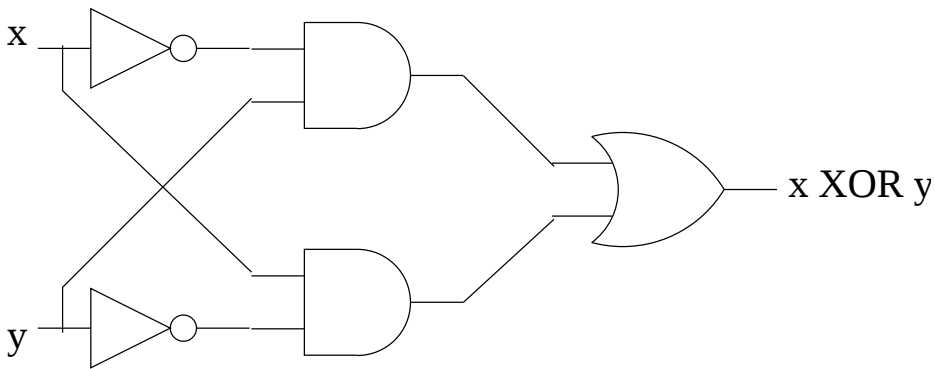


Some gates can have *more than 2* inputs

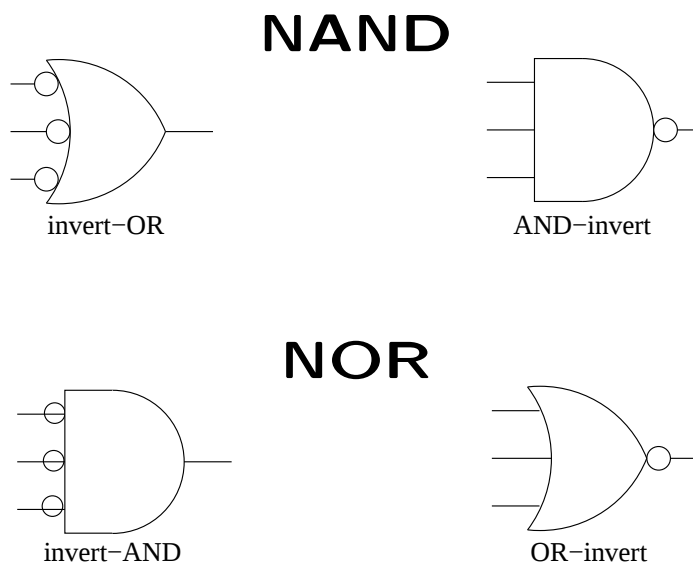

Logic Design and Analysis


Design Realize the logic circuit corresponding to a given function
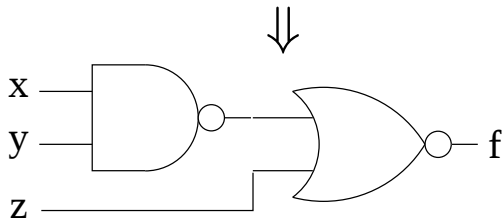
$$f(x, y, z) = \overline{\overline{xy} + z}$$



The circuit may be further minimized if necessary

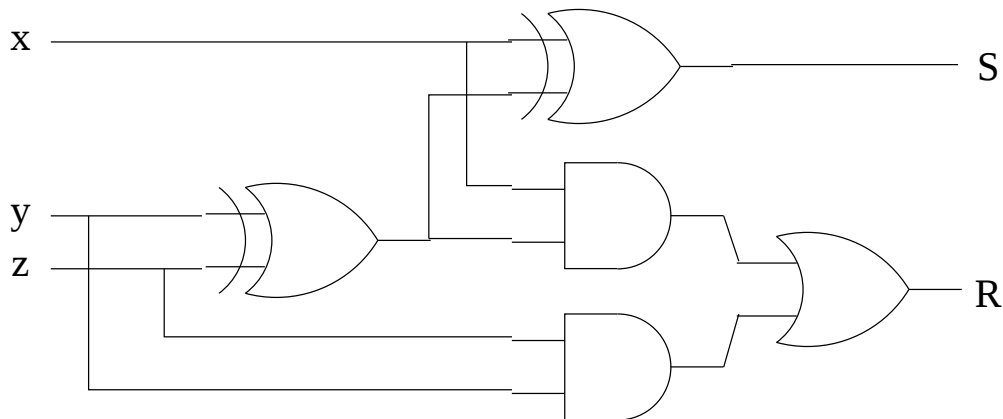Analysis Determine the logic function corresponding to a given circuit



⇓

$$f(x, y, z) = (S, R) = (x \oplus y \oplus z, x(y \oplus z) + yz)$$


The function may be further minimized if necessary

Circuits with Universal Gates

NAND and NOR gates are *simpler* and *cheaper* than NOT, AND, OR gates


NAND Circuits

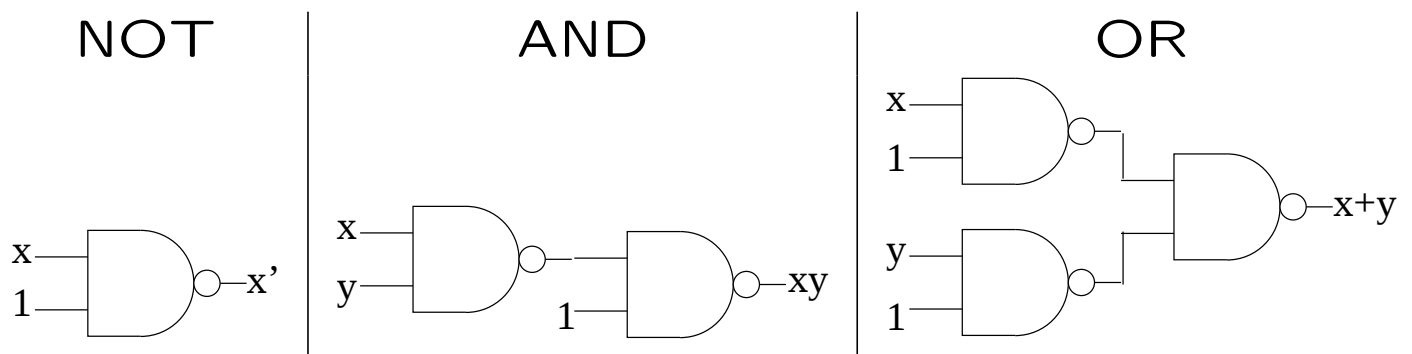(Better for implementing SOP expressions)



NOR Circuits

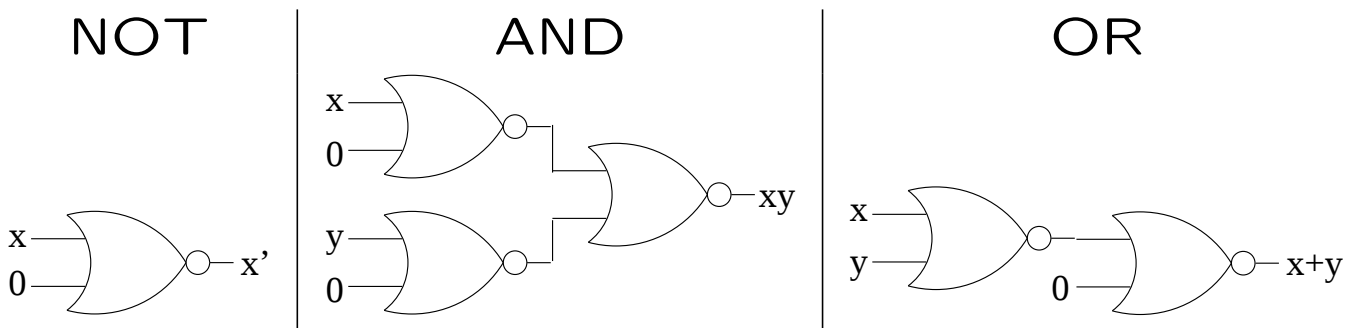(Better for implementing POS expressions)



Implementations with NAND Gates

SOP expression

$$\begin{aligned}f(a, b, c, d) &= a\bar{b} + \bar{a}c + d \\&= \overline{\overline{a\bar{b} + \bar{a}c + d}} \\&= \overline{\overline{a\bar{b}} \cdot \overline{\bar{a}c} \cdot \bar{d}} \\&= \overline{\overline{a\bar{b}} \uparrow \overline{\bar{a}c} \uparrow \bar{d}} \\&= (a \uparrow \bar{b}) \uparrow (\bar{a} \uparrow c) \uparrow \bar{d} \\&= (a \uparrow (b \uparrow 1)) \uparrow ((a \uparrow 1) \uparrow c) \uparrow (d \uparrow 1)\end{aligned}$$

POS expression

$$\begin{aligned}g(a, b, c, d) &= (a + \bar{b})(\bar{a} + c)d \\&= \overline{\overline{a + \bar{b}} \cdot \overline{\bar{a} + c} \cdot \bar{d}} \\&= \overline{\overline{a}\bar{b} \cdot \overline{\bar{a}c} \cdot d} \\&= \overline{(\bar{a} \uparrow b)(a \uparrow \bar{c})d} \\&= \overline{(\bar{a} \uparrow b)(a \uparrow \bar{c})d} \\&= \overline{(\bar{a} \uparrow b) \uparrow (a \uparrow \bar{c}) \uparrow d} \\&= ((\bar{a} \uparrow b) \uparrow (a \uparrow \bar{c}) \uparrow d) \uparrow 1 \\&= (((a \uparrow 1) \uparrow b) \uparrow (a \uparrow (c \uparrow 1))) \uparrow d) \uparrow 1\end{aligned}$$

Implementations with NOR Gates

SOP expression

$$\begin{aligned}f(a, b, c, d) &= a\bar{b} + \bar{a}c + d \\&= \overline{\overline{a\bar{b}}} + \overline{\overline{\bar{a}c}} + d \\&= \overline{\overline{a} + b} + \overline{a + \bar{c}} + d \\&= (\bar{a} \downarrow b) + (a \downarrow \bar{c}) + d \\&= \overline{(\bar{a} \downarrow b) + (a \downarrow \bar{c}) + d} \\&= \overline{(\bar{a} \downarrow b) \downarrow (a \downarrow \bar{c}) \downarrow d} \\&= ((\bar{a} \downarrow b) \downarrow (a \downarrow \bar{c}) \downarrow d) \downarrow 0 \\&= (((a \downarrow 0) \downarrow b) \downarrow (a \downarrow (c \downarrow 0))) \downarrow d) \downarrow 0\end{aligned}$$

POS expression

$$\begin{aligned}g(a, b, c, d) &= (a + \bar{b})(\bar{a} + c)d \\&= \overline{\overline{(a + \bar{b})(\bar{a} + c)d}} \\&= \overline{a + \bar{b} + \bar{a} + c + \bar{d}} \\&= \overline{a + \bar{b} \downarrow \bar{a} + c \downarrow \bar{d}} \\&= (a \downarrow \bar{b}) \downarrow (\bar{a} \downarrow c) \downarrow \bar{d} \\&= (a \downarrow (b \downarrow 0)) \downarrow ((a \downarrow 0) \downarrow c) \downarrow (d \downarrow 0)\end{aligned}$$